



**TÉCNICO**  
LISBOA

# MIRCROELETRONICS

## 3RD LAB REPORT

---

### Current Mirror Design

---

#### Authors:

Ana Beatriz Duarte (100747)  
Catarina Manuel (99903)  
Inês Castro (100318)

[beatriz.quirino.rosa@tecnico.ulisboa.pt](mailto:beatriz.quirino.rosa@tecnico.ulisboa.pt)  
[catarina.manuel@tecnico.ulisboa.pt](mailto:catarina.manuel@tecnico.ulisboa.pt)  
[ines.pires.e.castro@tecnico.ulisboa.pt](mailto:ines.pires.e.castro@tecnico.ulisboa.pt)

Group 7 — Shift L06  
2022/2023 — 2<sup>nd</sup> Semester, P4

# Contents

<b>1</b>	<b>Introduction</b>	<b>2</b>
<b>2</b>	<b>Theoretical Preparation</b>	<b>3</b>
2.1	Current Mirror with two NMOS . . . . .	3
2.2	channel-length modulation . . . . .	5
<b>3</b>	<b>Current Mirror Schematic, Symbol and Simulation</b>	<b>7</b>
3.1	Neglecting Channel-Lenght Modulation . . . . .	7
3.1.1	DC Sweep . . . . .	8
3.1.2	Corner Analysis . . . . .	9
3.2	Analyzing channel-length modulation . . . . .	10
<b>4</b>	<b>Conclusion</b>	<b>12</b>
<b>5</b>	<b>Referências</b>	<b>13</b>

# 1 Introduction

"The current mirror is one of the most important building blocks of analog integrated circuits." (Sedra, Smith, 2015) In the third laboratory of Microeletronics, there are two main goals: the first one is to study the MOS transistor as a current source, and, for that, throughout this report, a circuit of a basic current mirror is analysed, as the transistor Q2 works like a current source; the second one is to understand the impact of a side-diffusion phenomenon, denominated **channel-length modulation**.

This lab report is divided in two main sections:

The first section is a theoretical preparation, in which is presented the circuit of a basic current mirror whose transistors are analysed according to their working regions and to their behavior towards the impact of channel-length modulation (*clm*). In one hand, it's studied their working-regions and their behavior without the influence of *clm*; in another hand, it's studied their working regions and their behavior with the effect of *clm*. This study is associated with equations that guide, mathematically, the transistors characteristics.

The second section is a *Cadence virtuoso* analysis, in which are presented the schematic, the symbol of the basic current mirror and its performed simulations. In this section, the proposed activity is completed, i.e. the following items are achieved:


- Assuming that the input current and the output current are the same (10uA), design the W and L of the NMOS transistors to have an overdrive voltage of 200mV;
- Simulate the current mirror with a DC sweep output voltage range of 0 to 3.3V with comments about the simulation results referring in particular to the overdrive voltage, to the  $V_{DS}$  that ensures the output current identical to the input current and to the channel-length modulation impact;
- Perform a corner analysis;
- Keeping the same W/L, simulate, for typical conditions, the current mirror with MOS transistors with  $L=0.35\mu\text{m}$ ,  $1\mu\text{m}$ ,  $4\mu\text{m}$  and comment the channel-length modulation impact of L.

Finally, a comparison between the theory and the simulation results is commented in the conclusion.

## 2 Theoretical Preparation
 
### 2.1 Current Mirror with two NMOS

The basic current mirror designed with two NMOS transistors it's shown in 1.



Basic MOSFET current mirror.

**Figure 1:** Design with two NMOS

The design starts with a complex circuit that is used to generate a stable reference current  $I_{REF}$ . In this case, the NMOS transistors are identical, meaning that  $I_o = I_{REF}$ , thus the circuit simply replicates or mirrors the reference current in the output terminal, hence **current mirror**.

The connection of  $Q_1$ 's and  $Q_2$ 's gates provides an output current  $I_o$  that is related to the reference current  $I_{REF}$ , whose relationship is solely determined by the geometries of the transistors, which makes it "a simple and attractive relationship".

The connection between the gate and the drain of  $Q_1$  implies that  $V_G = V_D$ . Considering that  $V_{GS} > V_t$ , through the equation

$$V_{DS} \geq V_{GS} - V_t \quad (1)$$

it's concluded that  $Q_1$  is in saturation's region. Therefore, the drain's current of  $Q_1$  is given by:

$$i_{DS1} = \frac{\mu C_{ox}}{2} \frac{W_1}{L_1} (V_{GS} - V_{th})^2 \quad (2)$$

If  $Q_2$  is to supply a constant-current output, it is essential that  $Q_2$  operates in saturation, like  $Q_1$ . To ensure that  $Q_2$  is saturated, the circuit to which the drain of  $Q_2$  is to be connected must establish a drain voltage  $V_o$  that satisfies the equation

$$V_o \geq V_{GS} - V_t \quad (3)$$

Equivalently, in terms of the overdrive voltage  $V_{OD}$  of  $Q_1$  and  $Q_2$ ,  $V_o \geq V_{OD}$ . Hence, the drain's current of  $Q_2$  is given by:

$$i_{DS2} = \frac{\mu C_{ox}}{2} \frac{W_2}{L_2} (V_{GS} - V_{th})^2 \quad (4)$$


Considering that both transistors gate's current is zero, it's concluded that:

$$I_{REF} = I_{DS1} \quad (5)$$

and

$$I_o = I_{DS2} \quad (6)$$

In both transistors, the characteristic  $i_D$  in function of  $v_{DS}$  is given by the following graph:

 

**Figure 2:** Working regions of the both transistor, until saturation

The triode region is satisfied for  $v_{DS} \leq V_{OD}$ .

The transition between triode and saturation regions is given by  $v_{DSsat} = V_{OD}$ . The saturation region is satisfied for  $v_{DS} \geq V_{OD}$ .


- Region A: Curve bends because the channel resistance increases with  $v_{DS}$ ;
- Region B: Almost a straight line with slope proportional to  $V_{OD}$ ;
- Region C: Current saturates because the channel is pinched off at the drain end, and  $v_{DS}$  no longer affects the channel. Along this area, the equation  $v_{GS} = V_t + V_{OD}$  is satisfied.

Note: As a way of comparing both characteristics (with and without impact of channel-length modulation), it is dashed with cyan blue the curve without the impact of clm and with darker blue is the curve being study in this subsection.

(Sedra, Smith, 2015)


## 2.2 channel-length modulation

The saturation-region develops, in both transistors, as a result of the channel being "pinched-off" at the end of the drain, shown in figure 3a. Unfortunately, the "pinching-off" doesn't mean that the drain-to-source voltage's influence is over. The channel is still affected by additional increases since the pinch-off point is getting closer to the source, shown in figure 3b.

 

**Figure 3:** Channel "Pinching-off"

In addition to 3b, as the channel pinch-off point moves slightly away from the drain, because  $V_{DS}$  increases beyond  $V_{DS_{sat}}$ , the effective channel length reduces by  $\Delta L$ , as shown in the figure below.

 

**Figure 4:** Channel length is affected

i.e. for high values of  $V_{GS}$  (voltages greater than  $V_{DS_{sat}}$ ), this side-diffusion phenomenon reduces the length of the channel:  $L_{eff} = L_{real} - \Delta L$ .

As a result, the saturation-region drain-current expression **must be adjusted**, taking into account the **channel-length modulation**.

By incorporating the incremental channel-length reduction, the  $i_D$  equation is now written as

$$i_{DS} = \frac{\mu C_{ox}}{2} \frac{W}{L - \Delta L} (V_{GS} - V_{th})^2 \quad (7)$$

which can also be written as

$$i_{DS} = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2 \left(1 + \frac{\Delta L}{L}\right) \quad (8)$$


and, since,  $\frac{\Delta L}{L} = \lambda V_{DS}$ , the equation results in

$$i_{DS} = \frac{\mu C_{ox} W}{2} \frac{V_{GS} - V_{th}}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) \quad (9)$$

It's possible to say that the channel-length modulation impact can be reduced by increasing the transistor length.

In fact, generally, a length  $L < 1\mu m$  has significant impact of channel-length modulation, hence, a length  $L \geq 1\mu m$  is recommended for all transistors in saturation. However, increasing the length to values higher than  $1\mu m$  has no significant benefit for channel-length modulation.

The transistor Q1 is always saturated, so the point where  $V_{DSsat} = V_{OD}$  is simultaneously the point where  $V_{DS}$  is equal to  $V_{GS}$  (intersection point), i.e.  $I_{REF} = I_{DS1}$  (shown in figure 2) However, in the transistor Q2 the point where  $V_{DS}$  is equal to  $V_{GS}$  (intersection point), i.e.  $I_{out} = I_{DS2}$  happens **after** the point  $V_{DSsat} = V_{OD}$  (saturation transition point), like is shown in the figure below.

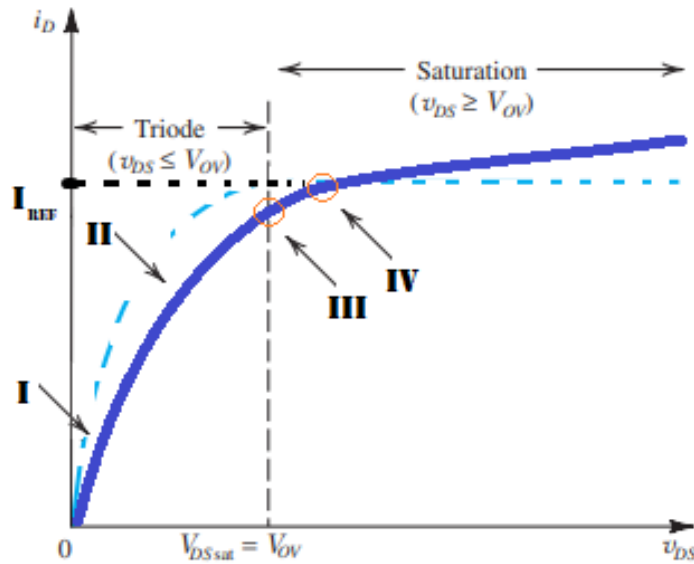

**Figure 5:** Working regions of the transistor Q2, with emphasis on the intersection point

The triode region is satisfied for  $v_{DS} \leq V_{OD}$ .

The transition between triode and saturation regions is given by  $v_{DSsat} = V_{OD}$ .

The saturation region is satisfied for  $v_{DS} \geq V_{OD}$ .


The regions I and II are similar to the the regions B and A, respectively, of fig 2.

- Region III: The transistor enters the saturation region, but  $V_{DS}$  is different than  $V_{GS}$ , so  $V_{GS}$  continues to increase;
- Region IV:  $V_{DS}$  is equal to  $V_{GS}$ , meaning that, only now,  $I_o = I_{DS2}$ .






The simulation schematic is shown in the figure bellow.

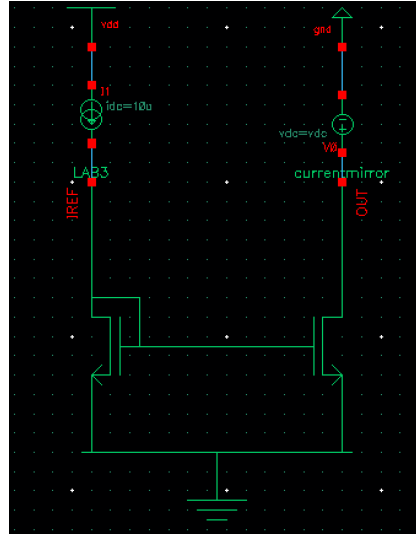

**Figure 7:** Simulation of the current mirror

### 3.1.1 DC Sweep

 

**Figure 8:** Cadence Virtuoso analyses: current mirror behavior, neglecting channel-length modulation; in pink, the output and in green, the input.

In this simulation,  $V_{DS}$  is varying between 0V and 3.3V (x axis) and the y axis corresponds to  $I_D$ .

It is possible to observe that  $I_D$  is nearly constant with the increase of  $V_{DS}$  in the zone of saturation, confirming that current mirrors are useful to copy current sources. This occurs when the value of  $V_{DS}$  of the two NMOS transistors is the same. Channel-length modulation is being neglected, this behavior is a result of the channel's length being  $100\mu m \gg 1\mu m$ . The value of  $I_D$  for the first NMOS stays constant, while the value of  $I_D$  for the second NMOS increases until it reaches a value of  $I_D$  equal to the one of the first NMOS, reaching saturation (for  $V_{DS}$  approximately equal to 0.42V), and having from then on a value of  $I_D$  approximately constant and equal to the first transistor ( $I_{OUT} = I_{REF}$ ). The  $V_{OD}$  initially is higher than the value of  $V_{DS}$ , being equal to the value of  $V_{DSsat}$  when the transistor reaches the zone of saturation, from then on the value of  $V_{OD}$  is lower than  $V_{DS}$ , since  $V_{DS}$  is continually increasing.

### 3.1.2 Corner Analysis

The corner analysis was then performed, for temperatures of  $-40^{\circ}\text{C}$  and  $125^{\circ}\text{C}$ . In the corner analysis, it is possible to observe that overall the same behaviour as described in the previous section was observed. Once more, the x axis corresponds to  $V_{DS}$  and the y axis to  $I_D$ .


 



Figure 9: Corner analysis

In the corner analysis with  $T=-40^{\circ}\text{C}$  (10a), the worst power and worst one (corners 0 and 4) reach saturation faster and maintain a slightly higher value of  $I_D$  than the other two corners (2 and 6 which correspond to worst speed and worst zero). This occurs, since  $V_{th}$  is higher for worst speed and worst zero, so a higher  $V_{GS}$  is needed to reach the same  $V_{OD}$  as the other two corners, this leads to a higher value of  $V_{DS}$  needed to reach saturation. It is possible to observe that worst power and worst one (corners 0 and 4) reach saturation approximately at the same time, but worst power reaches it slightly faster. For worst speed and worst zero, worst speed reaches saturation faster.

 The same behaviours for  $T=-40^{\circ}\text{C}$  occur to  $T=125^{\circ}\text{C}$  (10b), where worst power, worst speed, worst one and worst zero correspond to corners 1, 3, 5 and 7 respectively. The line that stays constant corresponds to  $I_{REF}$  of the first NMOS.



(a) For  $T=-40^{\circ}\text{C}$

 


(b) For  $T=125^{\circ}\text{C}$

Figure 10: Corner analysis


Comparing the two temperatures, for  $125^{\circ}\text{C}$  the value of  $V_{th}$  is lower, so the corners for this temperature reach saturation faster than for  $T=-40^{\circ}\text{C}$  which has a higher value of  $V_{th}$ .

### 3.2 Analyzing channel-length modulation


In this analysis, the value of length was changed to  $0.35\mu m$ ,  $1\mu m$  and  $4\mu m$ , without altering  $\frac{W}{L}$ , so the width was also changed to prevent the alteration of this ratio.

 

**Figure 11:** Cadence Virtuoso analyses: current mirror behavior, including channel-length modulation, with transistor length  $L = 0.35\mu m$  ; in pink, the output and in green, the input.

 

**Figure 12:** Cadence Virtuoso analyses: current mirror behavior, including channel-length modulation, with transistor length  $L = 1\mu m$  ; in pink, the output and in green, the input.

 

**Figure 13:** Cadence Virtuoso analyses: current mirror behavior, including channel-length modulation, with transistor length  $L = 4\mu m$  ; in pink, the output and in green, the input.

The value where the input and output lines intersect is when  $I_{OUT} = I_{REF}$ , so, when both transistors have the same value of  $V_{DS}$ . For  $L = 0.35\mu m$ , this value is around  $772mV$ , for  $L = 1\mu m$  is  $810mV$  and for  $L = 4\mu m$  is  $792mV$ , so this value is around  $0.8V$ . It is important to recall that, in the second transistor,  $V_{OD} = V_{GS} - V_{th} = V_{DS}$  when entering the saturation region, but, because of channel-length modulation, for  $I_{OUT} = I_{REF}$ ,  $V_{GS}$  still needs to increase so that it can reach the same value as  $V_{DS}$  (and then all voltages became the same for both transistors, and so the currents too). This value when  $V_{DS} = V_{GS}$  is around  $0.8V$ , as simulated. It is also possible to withdraw from the graphics that, for different lengths, the slope in the saturation region differs, which is also because of channel-length modulation. To analyse this behavior, the channel-length modulation coefficient  $\lambda$  was calculated using the derivative of the equation 9 in function of  $V_{DS}$  obtaining:

$$\frac{di_{DS}}{dV_{DS}} = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2 \lambda \quad (12)$$

Since,  $\mu C_{ox} = 170\mu A/V^2$ ,  $\frac{W}{L} = 2.94$ ,  $V_{GS} - V_{th} = V_{OD} = 200mV$ , but the value of  $\frac{di_{DS}}{dV_{DS}}$  is still needed, to obtain this value the slope of the graph after  $I_{OUT} = I_{REF}$  was obtained. For  $L = 0.35\mu m$  it is approximately  $1.24\mu A/V$ ,  $0.2284\mu A/V$  for  $L = 1\mu m$  and for  $L = 4\mu m$  is  $0.1746\mu A/V$ . Isolating  $\lambda$  in the previous equation, the values obtained for the channel-length modulation coefficient are  $0.125$  for  $L = 0.35\mu m$ ,  $0.0229$  for  $L = 1\mu m$  and  $0.0175$  for  $L = 4\mu m$ . The results obtained are the expected, for the lower value of length ( $L = 0.35\mu m$ ) the value obtained for the channel-length modulation coefficient is higher than for the other lengths, and the difference in the channel-length modulation coefficient for the other two lengths is very small, which shows that for lengths  $L > 1\mu m$   $\lambda$  has less influence in  $I_D$ .

Furthering the analyses, it is clear that channel-length modulation affects  $I_D$  significantly for length values below  $1\mu m$ . It is also clear that increasing the channel's length mitigates channel-length modulation, because  $\Delta L$  is diluted in bigger lengths and so causes less impact. So, for  $L < 1\mu m$  the channel-length coefficient  $\lambda$  is bigger and  $I_D$  varies more; for  $L > 1\mu m$ ,  $\lambda$  is smaller, decreases with the increase of  $L$  and  $I_D$  varies less.

## 4 Conclusion

Throughout the third lab report, it was intended to study the transistor as a current source and, for that, it's analysed a current mirror circuit.

The first part, was written a theoretical preparation about the current mirror circuit, in which the transistor Q2 works like a current source. In this part, it was able to understand the effects of the channel-length modulation, which were explored further in the second main part of the report.

The second part, it was given a deep dive analysis to the simulations performed to the current mirror circuit, projected in *Cadence virtuoso*. In this analysis it was possible to observe that when neglecting channel-length modulation coefficient, the second NMOS reaches saturation for  $V_{OD} = V_{DS}$ , in this case  $I_{OUT} = I_{REF}$  and both transistors have the same  $V_{DS}$ , this occurs for length values very superior to  $1\mu m$ , as one was expecting to occur theoretically. However, for different values of length one observed the effect of channel-length modulation coefficient. For lower values of length (less than  $1\mu m$ ) the effect of this coefficient was more present, in this cases the NMOS transistor reached saturation for  $V_{OD} = V_{DS}$ , but it was still needed an increase in  $V_{GS}$  to obtain  $I_{OUT} = I_{REF}$ , so after reaching saturation  $I_{DS}$  doesn't stay approximately constant. It was also possible to understand that, experimentally, the value of  $I_{OUT} = I_{REF}$  does not stay always constant, not even when neglecting channel-length modulation coefficient as one would expect from the theoretical models. In the corner analysis, one can understand that for  $T=125^{\circ}C$  the saturation region is reached faster than for  $T=-40^{\circ}C$ , since the value of  $V_{th}$  is higher for  $T=-40^{\circ}C$ . It was also possible to conclude that the corners with lower  $V_{th}$  reach saturation faster.

As the group was able to reach the settled goals, the third lab of Microeletronics is completed successfully.

## 5 Referências

- [1] R. J. Baker, "CMOS: Circuit Design, Layout, and Simulation", 3rd edition, 2010.
- [2] Adel S. Sedra, Kenneth C. Smith, "Microelectronic Circuits", 7th edition, p.257-258, p.271, p.509, p.513, 2015.
- [3] "0.35  $\mu$ m CMOS C35 Process Parameters", Document Number: ENG -182, Revision: 2.0
- [4] Robert Keim, "MOSFET Channel-Length Modulation", 2016. Visited in 26/5/23:  
<https://www.allaboutcircuits.com/technical-articles/mosfet-channel-length-modulation/>